






life.augmented

Active inrush current limiter based on SCRs for 3.6kW bridgeless totem pole PFC

- **ST AC-DC inrush current limiter solutions**
- PFC totem pole topology using SiC MOSFETs and thyristors
- Evaluation board performance
- Takeaways

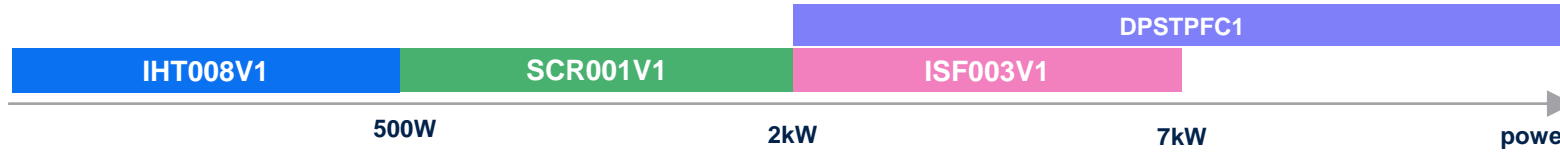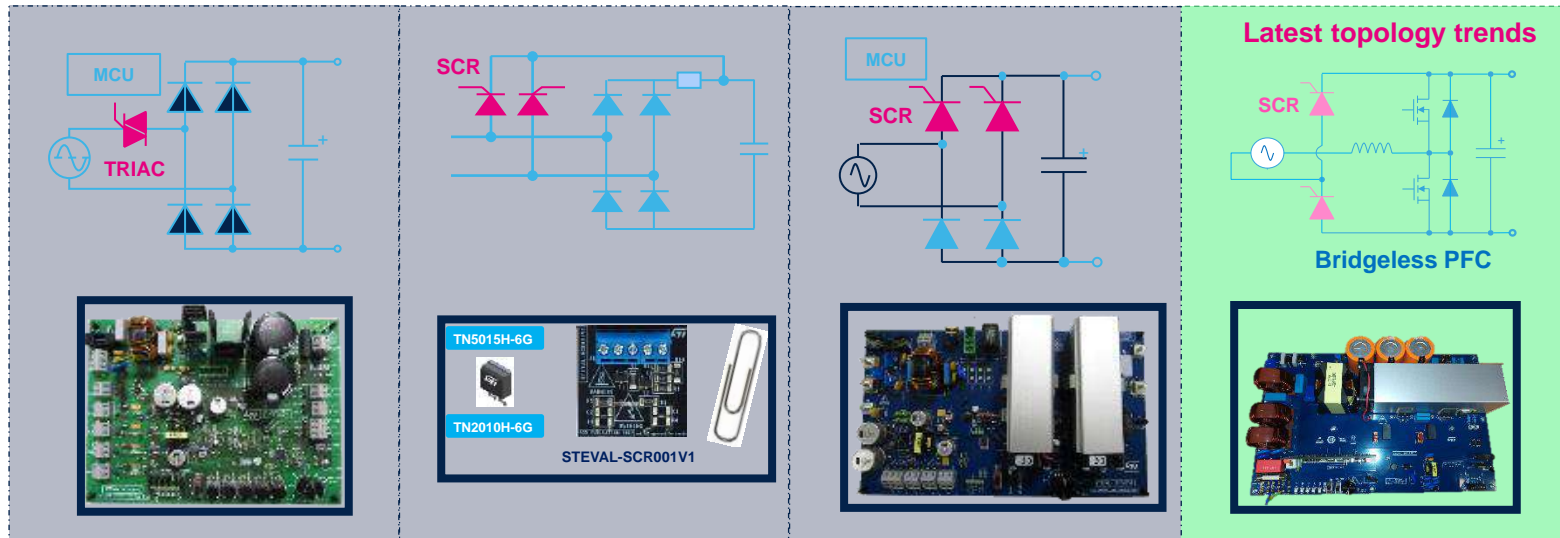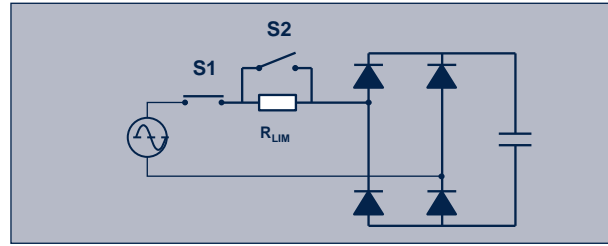ST AC-DC inrush current limiter solutions



SMART

- Programmable soft power up control
- Controlled multiple peak current limitation
- Zero-current Switch

SAFETY

- No Contact Bounce: no spark, no EMI
- Faster line-drop recovery
- Increase switching life expectancy

COMPACT

Low profile design, smaller height thanks to D²PAK package


Agenda

- ST AC-DC inrush current limiter solutions
- **PFC totem pole topology using SiC MOSFETs and thyristors**
- Evaluation board performance
- Takeaways


PFC totem pole topology (1/5)

Traditional PFC totem pole



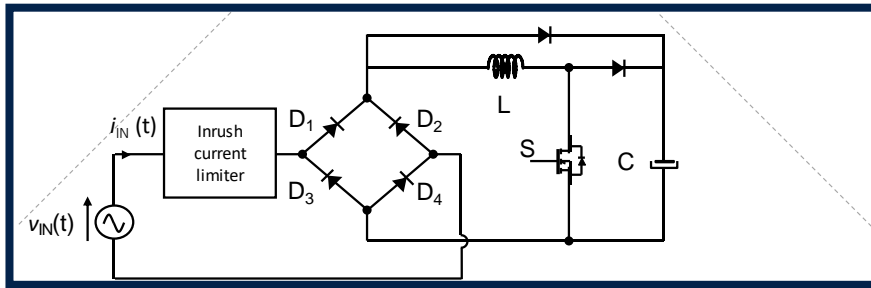
- A conventional PFC circuit:
 - Consists of a full bridge rectifier and a boost pre-regulator
 - A large portion of system losses are in the diode bridge



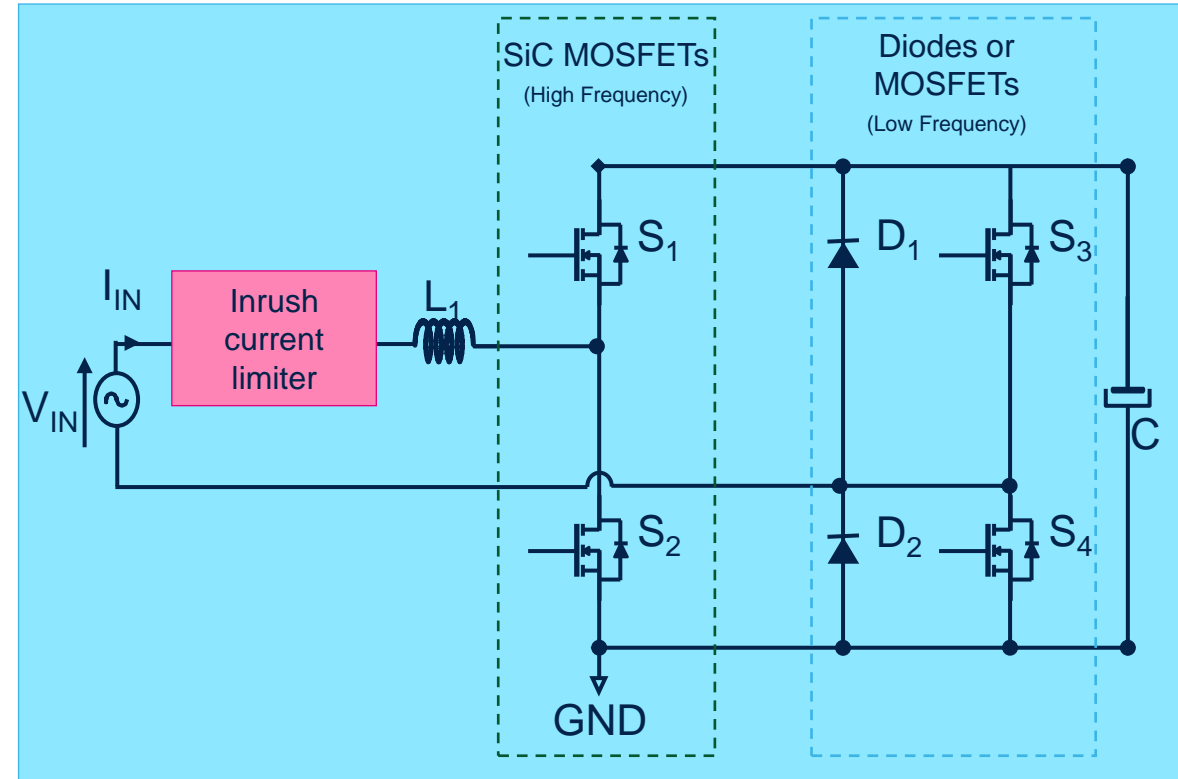- In a traditional totem pole PFC:
 - The diode losses are eliminated
 - Low frequency switches are diodes or MOSFETs
 - Needs an Inrush current limiter (NTC + relays)




PFC totem pole topology (2/5) Operation

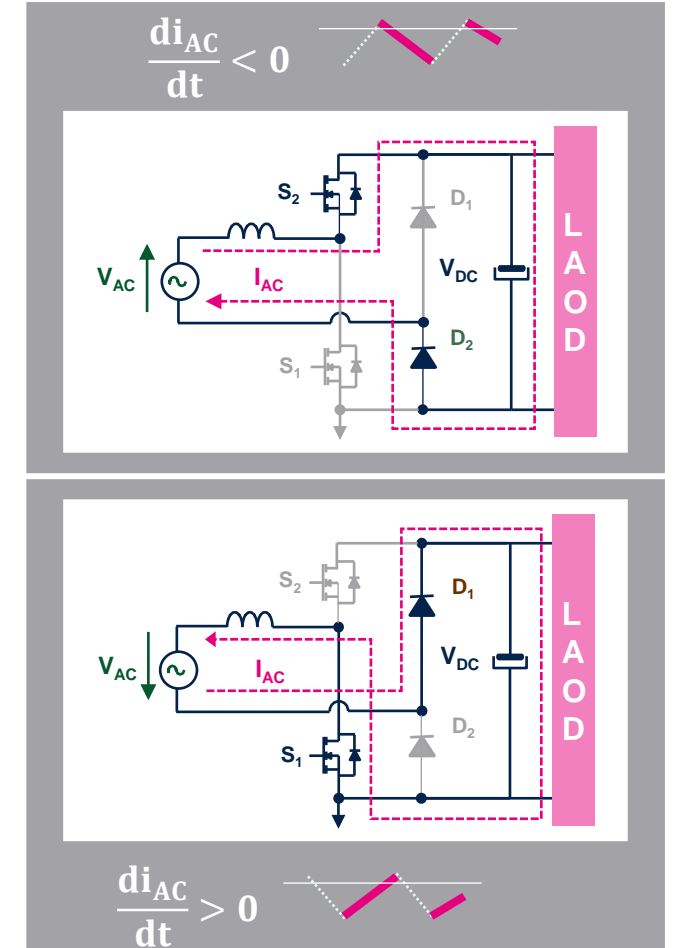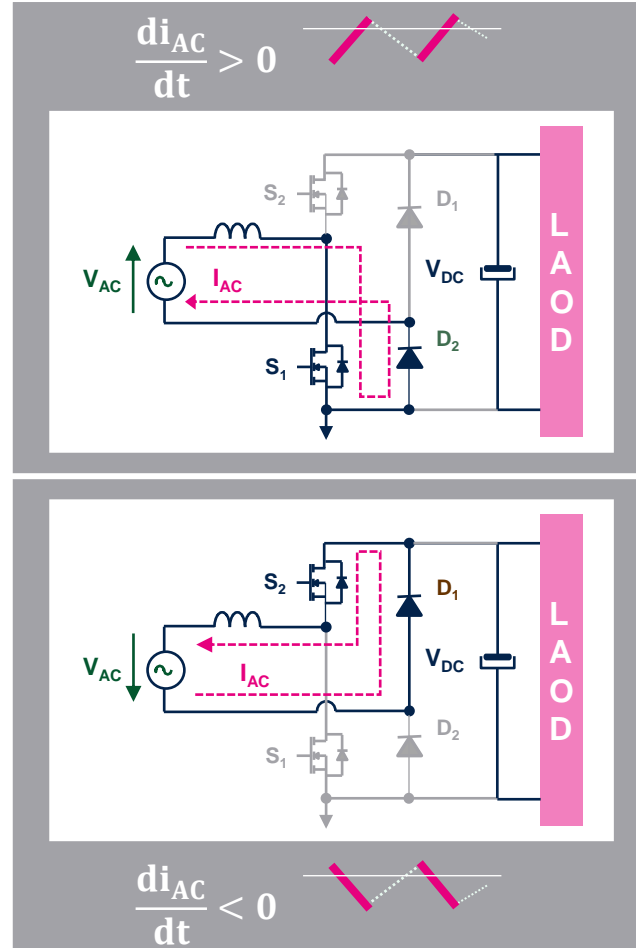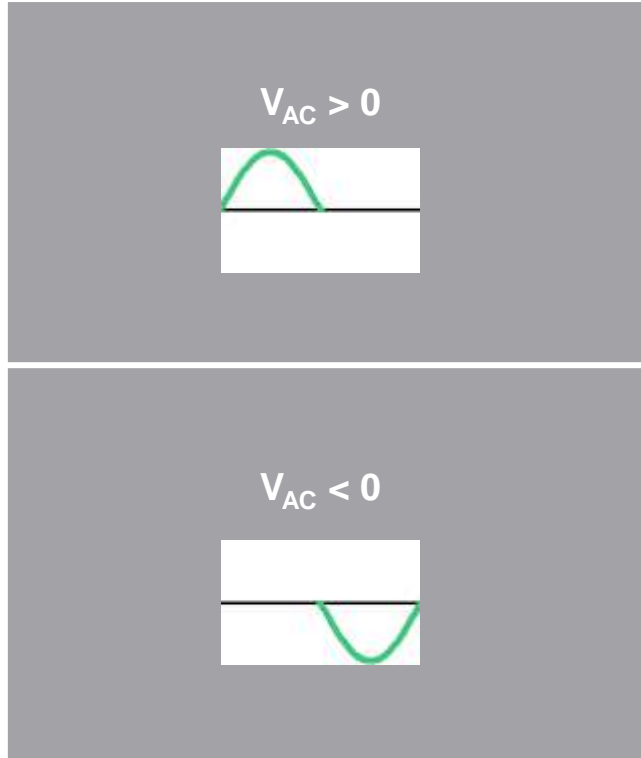


- D1 /D2 diodes (can be replaced by MOSFETs) works at AC line frequency
 - Needs an Inrush current limiter (NTC and Relay)
- } SCRs solution

PFC totem pole topology (3/5)

SCRs phase control

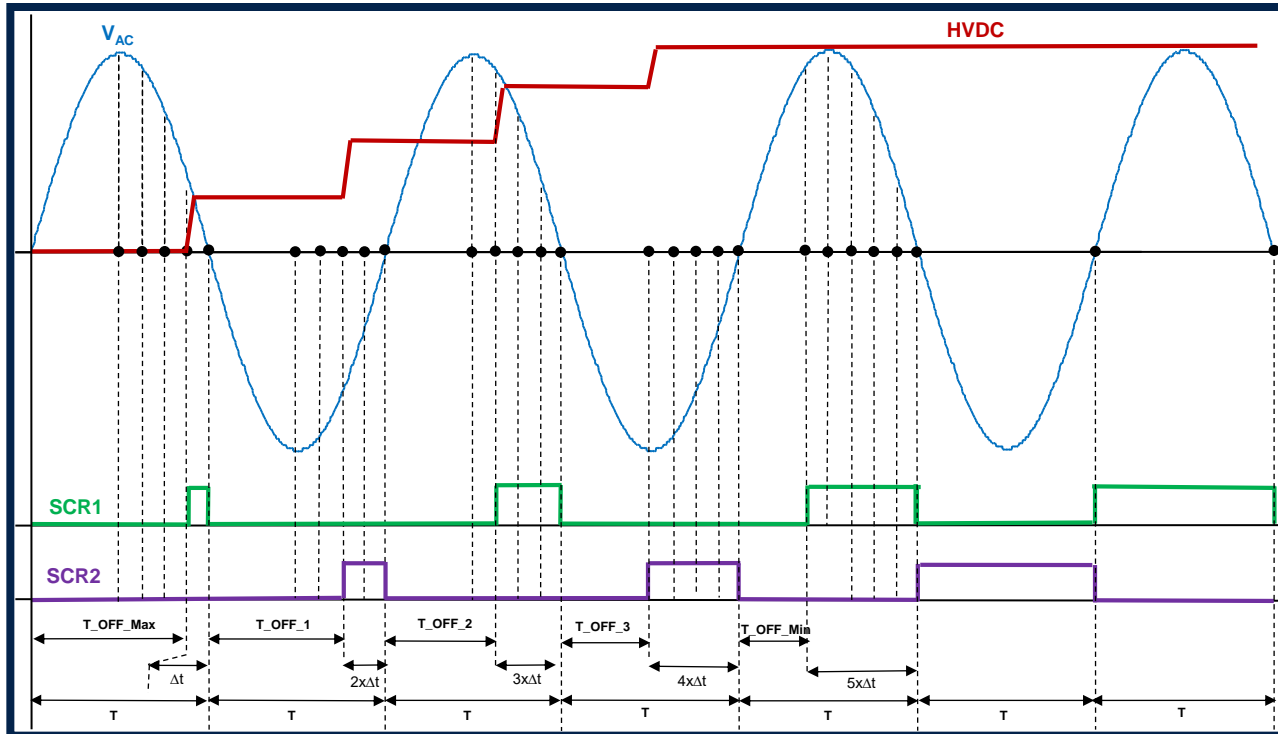


- Bulk capacitor is charged according to time-dependent pulse train driving SCR1 and SCR2
- SCR1 and SCR2 are synchronized according to the zero crossing (ZVS) of the AC line
- SCR1 and SCR2 are alternatively controlled according to the AC line polarity by reducing the turn-on delay ("T_OFF") by a constant Δt at each half AC line cycle
- SCR1 and SCR2 are controlled by phase angle up to the turn-on delay ("T_OFF") is lower than "T_OFF_Min"

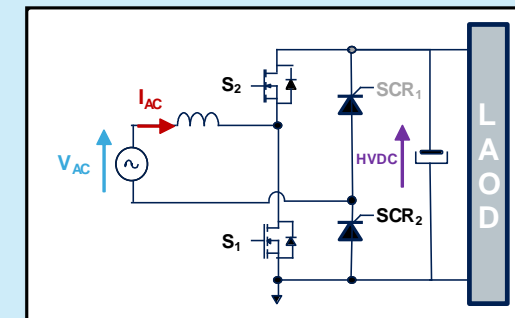


- Control the inrush-current to charge a DC bus capacitor
- Disconnect the DC bus capacitor from the AC mains when it does not have to operate

PFC totem pole topology (4/5) MOSFET vs SCR comparison

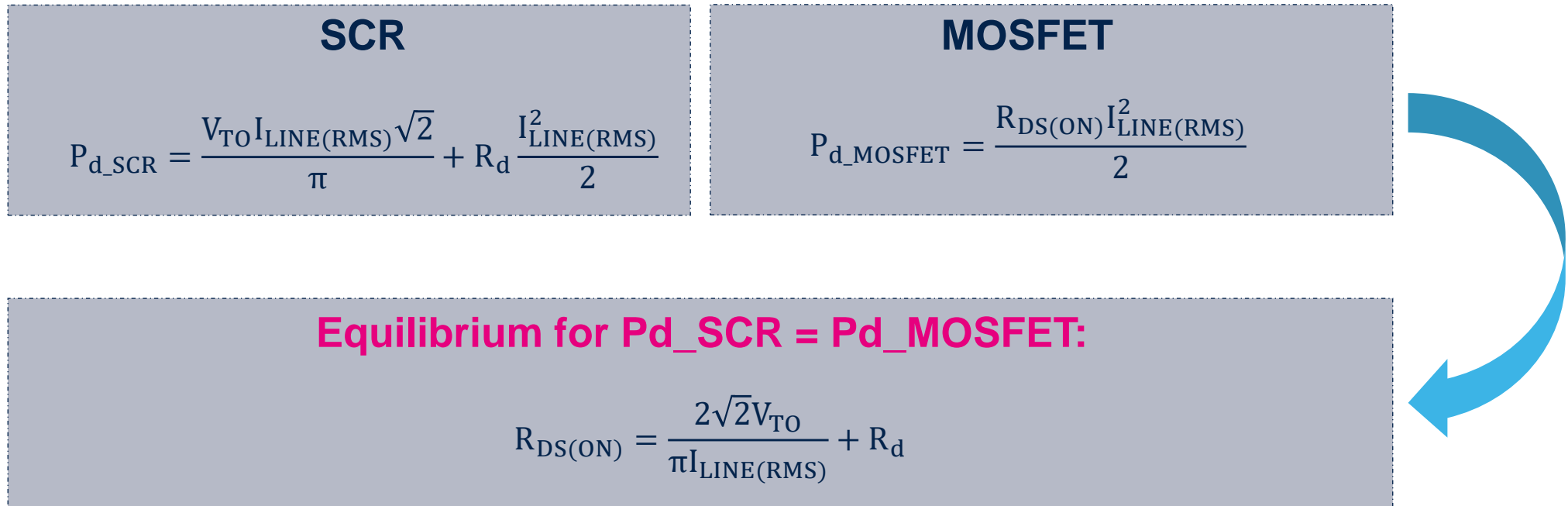As low frequency switching, only the conduction losses are considered




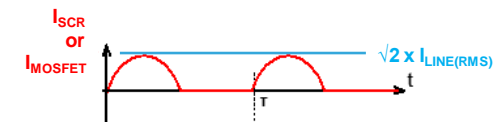Note: losses are calculated for single half-wave conduction (so for each device).
Multiply by 2 to calculate the total losses (for the 2 SCR or the 2 MOS).



PFC totem pole topology (5/5) MOSFET vs SCR comparison

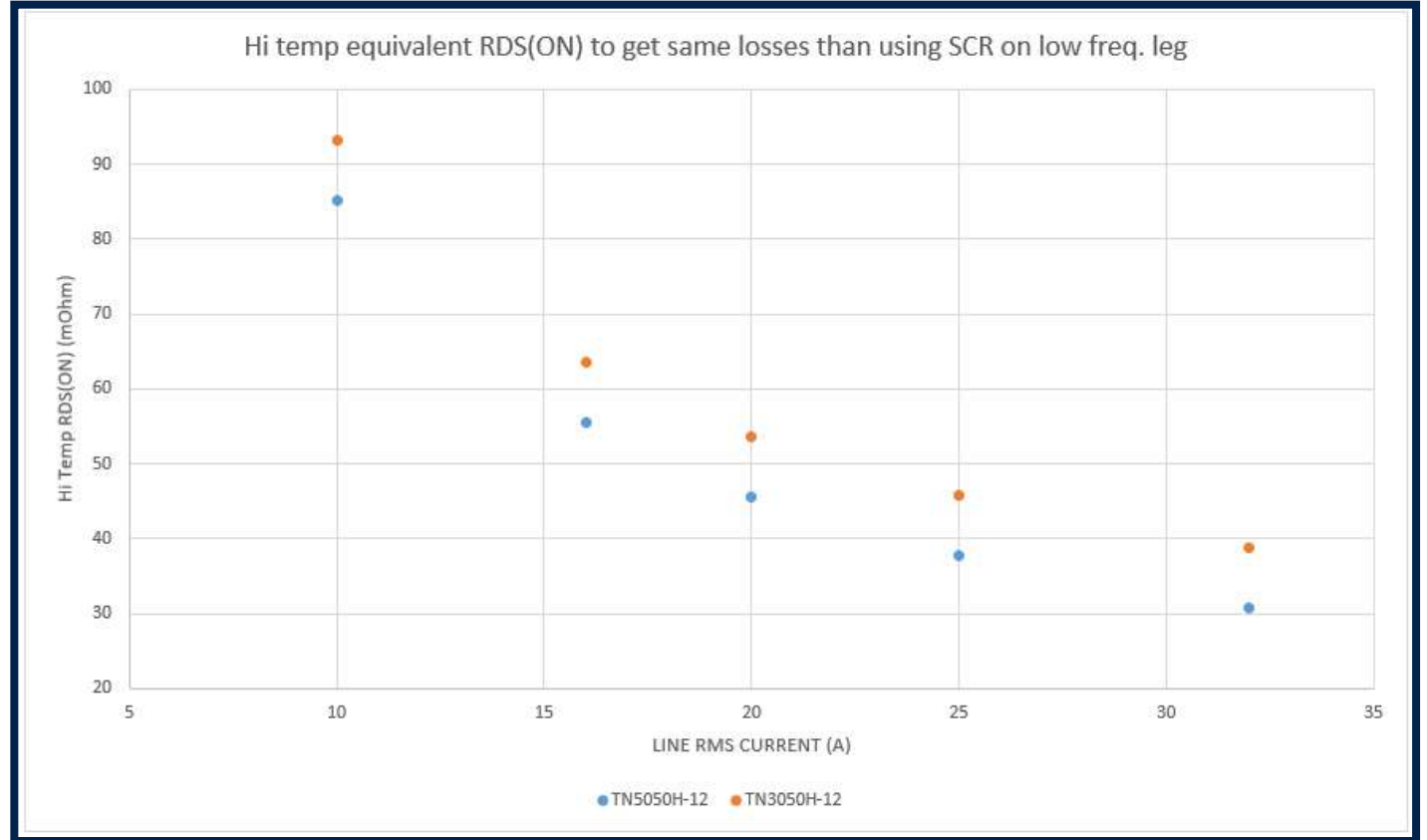- SCR have the same efficiency as MOSFET but with a silicon area more optimized
- With the traditional NTC / Relay solution, the contact resistance relay is needed to be into account
- SCRs surge current capabilities makes the SCR the ideal candidate for bridge applications where the devices can be submitted to voltage surges




Agenda


- ST AC-DC inrush current limiter solutions
- PFC totem pole topology using SiC MOSFETs and Thyristors
- **Evaluation board performance**
- Takeaways

Evaluation board performance

Design content

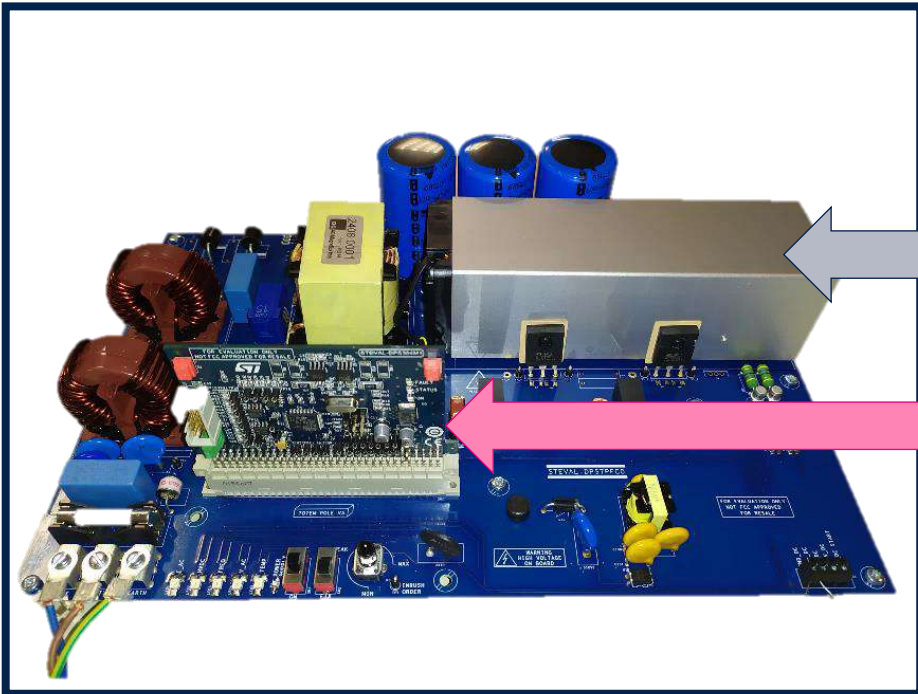


Reference	Name	Description
STEVAL-DPSTPFC0	AC - DC power board	Bridgeless Totem Pole boost with auxiliary supply
STEVAL-DPS334M1	PFC control board	32-bit MCU control board
STEVAL-DPSADP01	Adapter Board	Interface for MCU debugging and USART communication

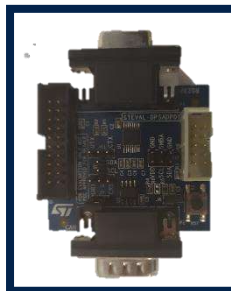

Evaluation board performance


Firmware overview

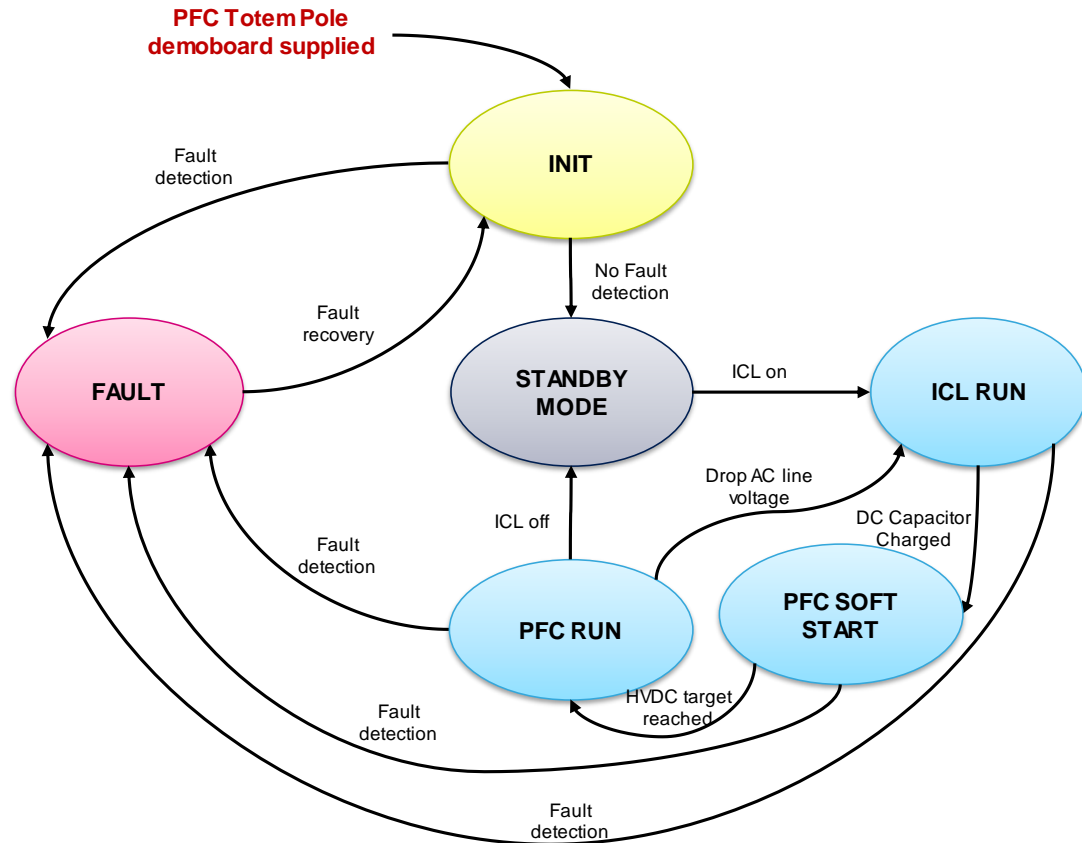

- Control loop:
 - Average current-mode control method I
 - Continuous and discontinuous conduction mode
- Outer voltage loop performed at 72 kHz
- Outer voltage loop performed at 2 times of AC line frequency
- DFF is used to pre-calculate a duty ratio and to improve the transient response
- Digital average current mode control in CCM and DCM including:
 - Bus voltage and AC line currents sampling
 - Voltage error calculation
 - Voltage PI regulation
 - Reference current calculation
 - Current error calculation
 - Duty cycle feed-forward generation
 - Final duty cycle computation


Evaluation board performance

PFC totem pole start-up

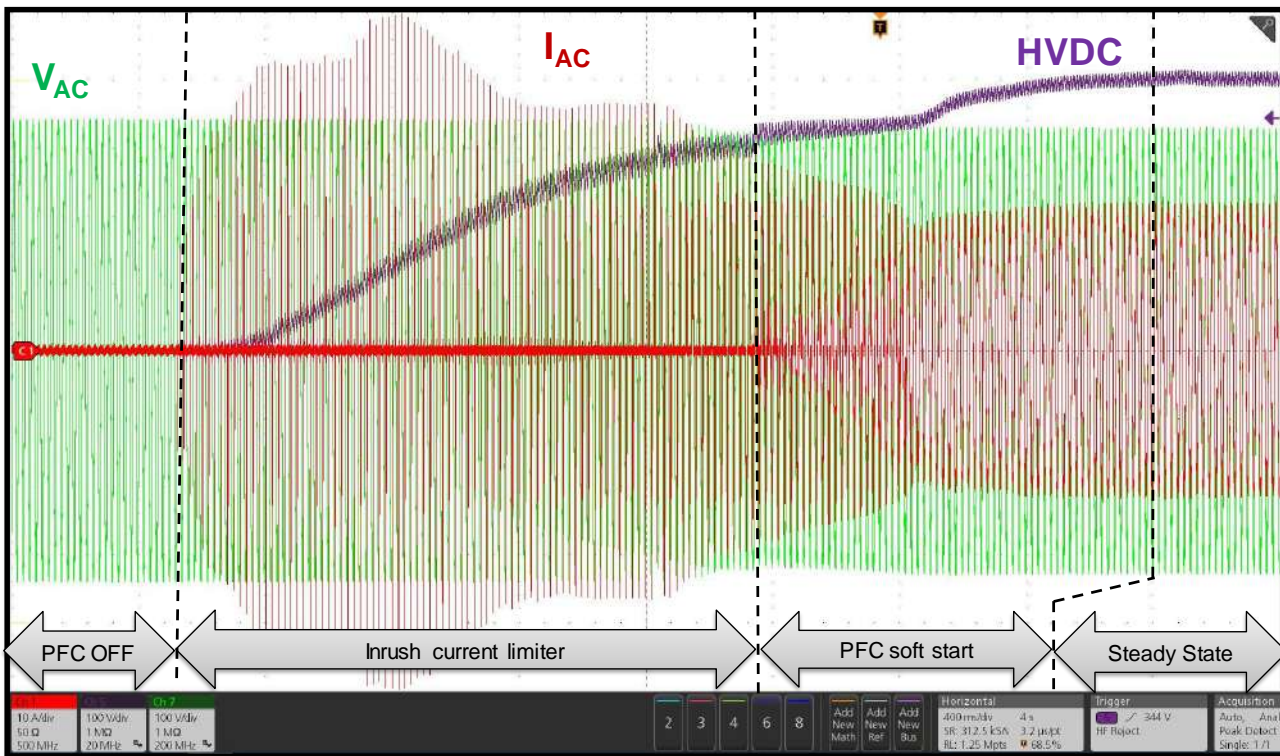


To ensure a smooth PFC start-up a soft start routines has been implemented on the MCU firmware:

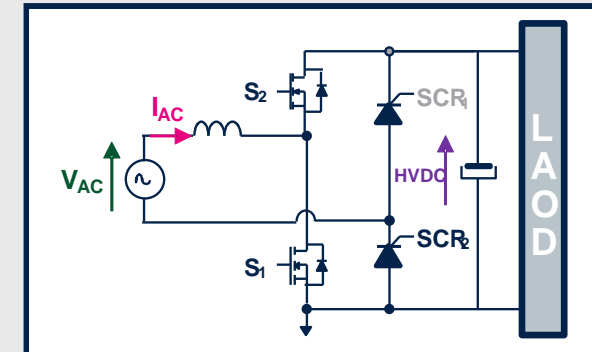- 1) **Inrush current limiter:** SCRs are controlled with a progressive phase control and the output capacitor can be smoothly up to the AC line peak voltage.
- 2) **PFC soft start:** The output voltage reference is controlled from AC line peak voltage to 400 Vdc with a smoothly voltage ramp.





Evaluation board performance PFC efficiency / THD measurement

VAC = 230 VRMS @ 50 Hz

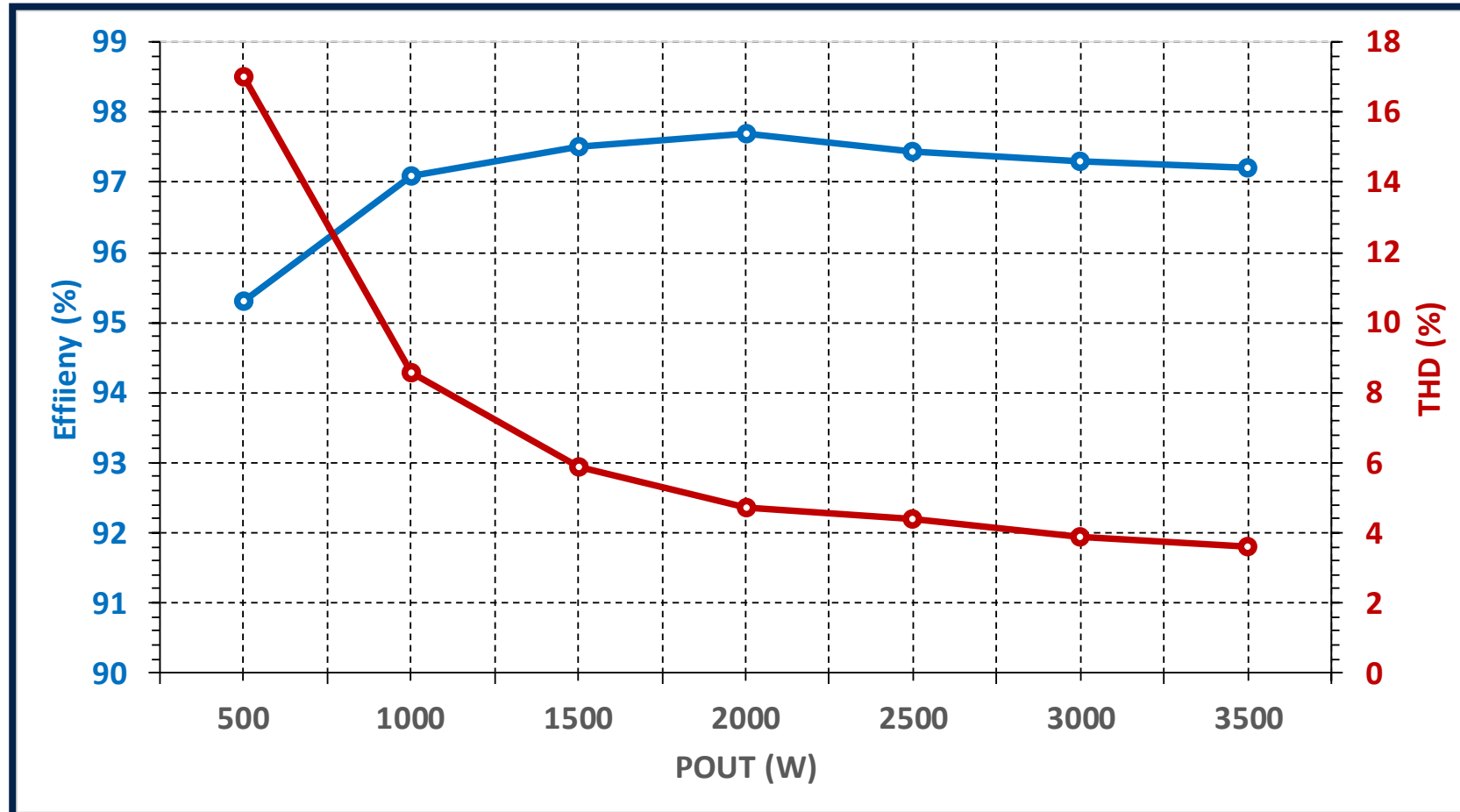


Evaluation board performance SiC MOSFET control

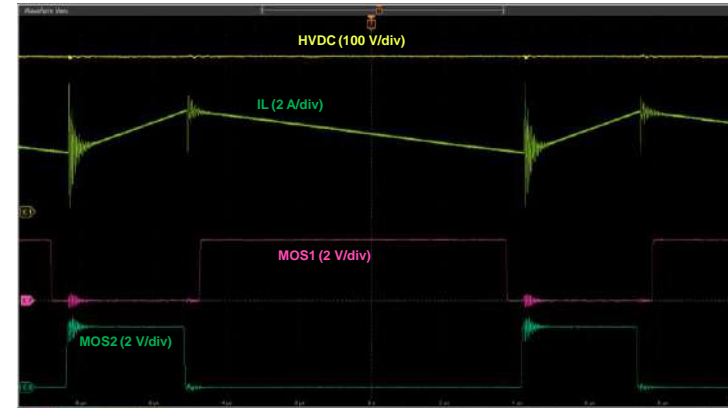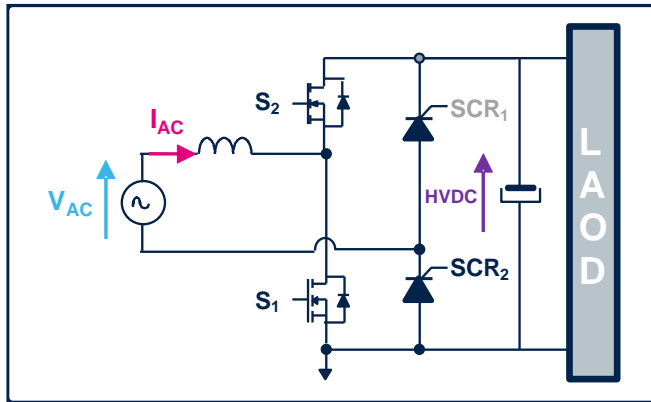- SiC MOSFETs are operating in synchronous conduction mode to improve efficiency



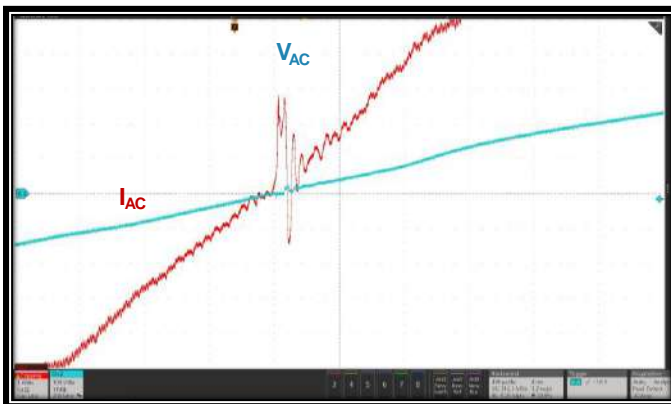- Current spike is generated at each AC line zero cross





- Duty ratio of switch changes abruptly from zero to almost 100% after each AC line zero cross
- High voltage is applied to the inductor (HVDC). A high positive current spike is generated
- Same phenomenon with diode or MOSFET

Evaluation board performance

SiC MOSFET control

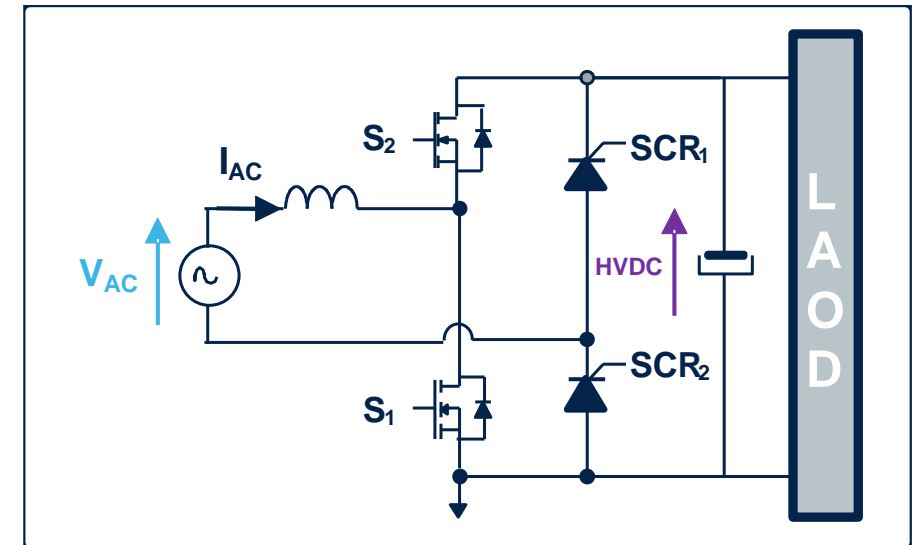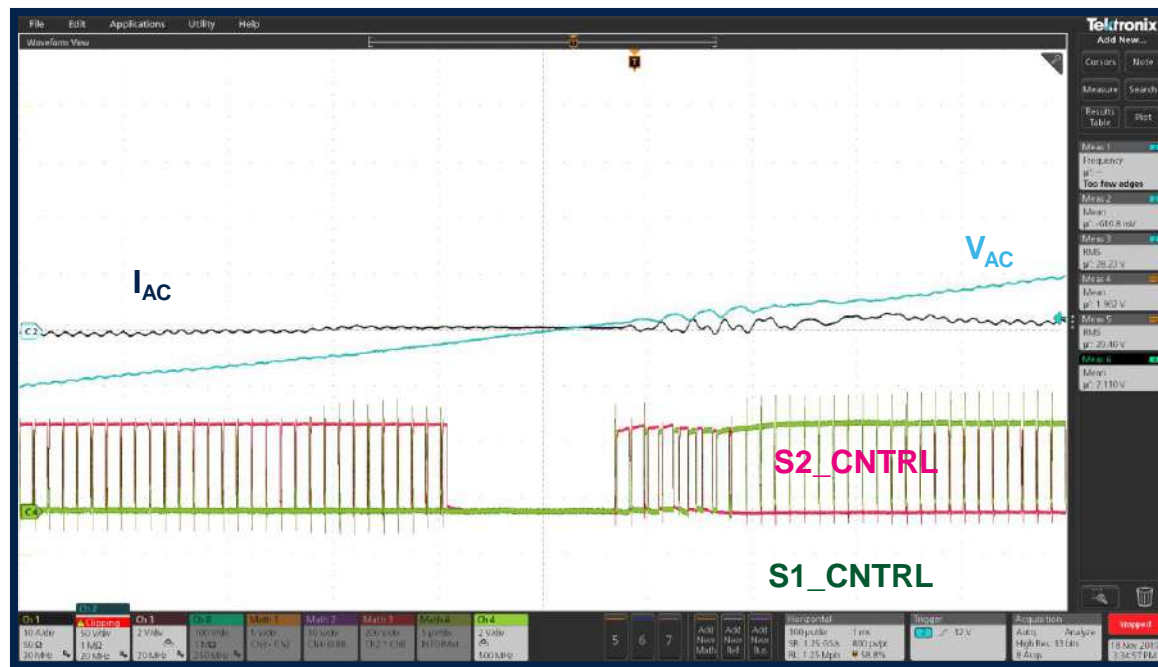
- SiC MOSFETs are controlled with a smart Duty Cycle control at each AC line zero cross
 - To reduce peak current through boost inductor at the AC line zero crossing
 - To improve common mode noise




Evaluation board performance

Common mode noise measurement (load = 800 W / 230 V_{RMS} / 50 Hz)

Without smart Duty cycle control

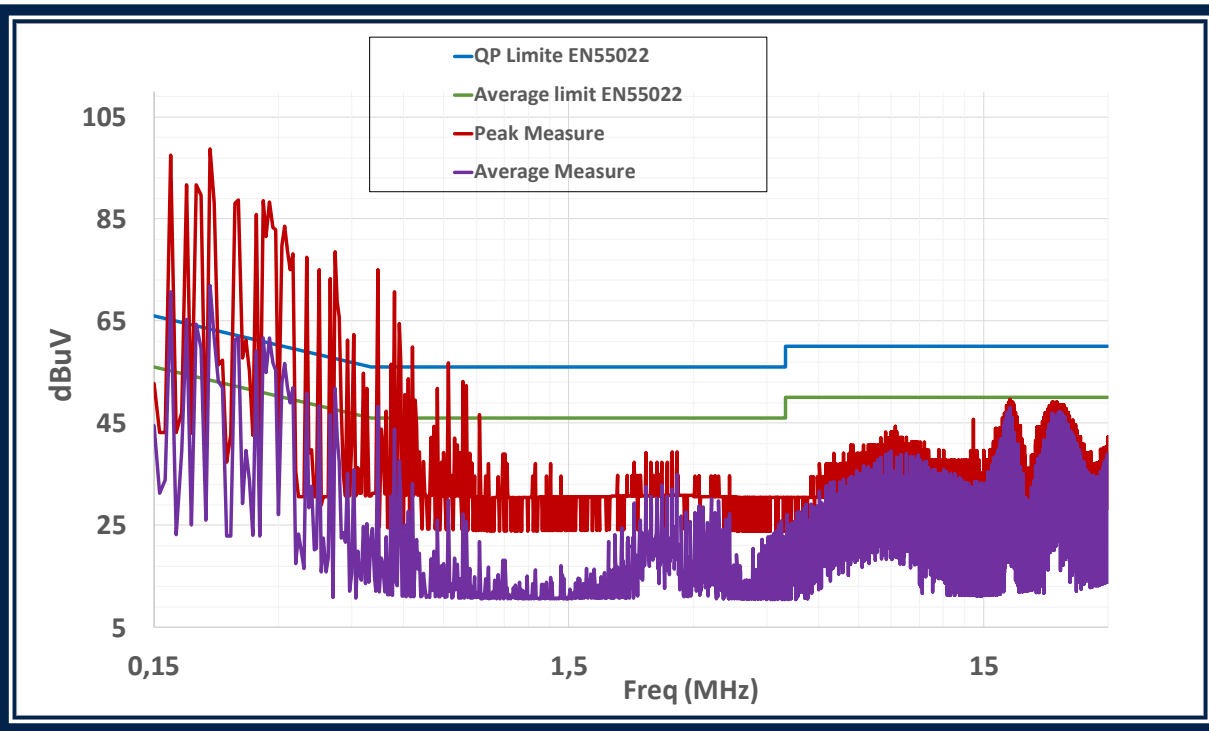


With smart Duty cycle control

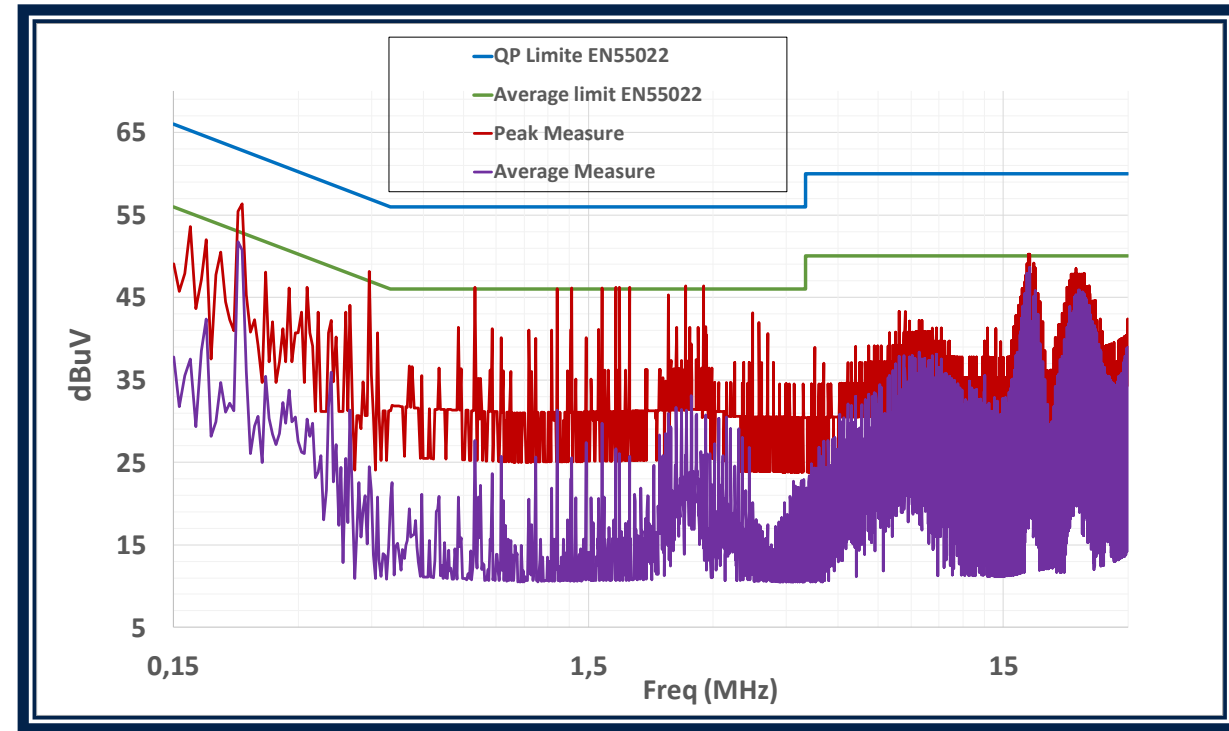


Evaluation board performance

Drop AC line voltage

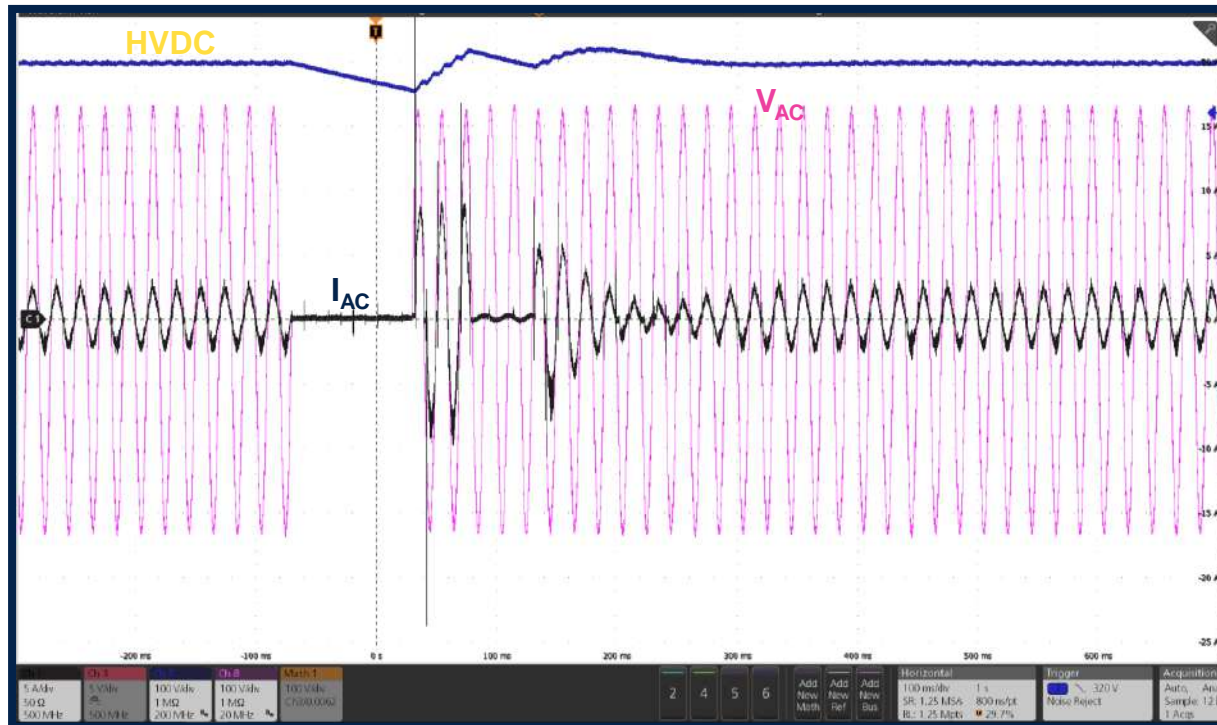AC line voltage interrupt lasts less than 30ms
SCRs and SiC MOSFETs are kept "ON", criteria A




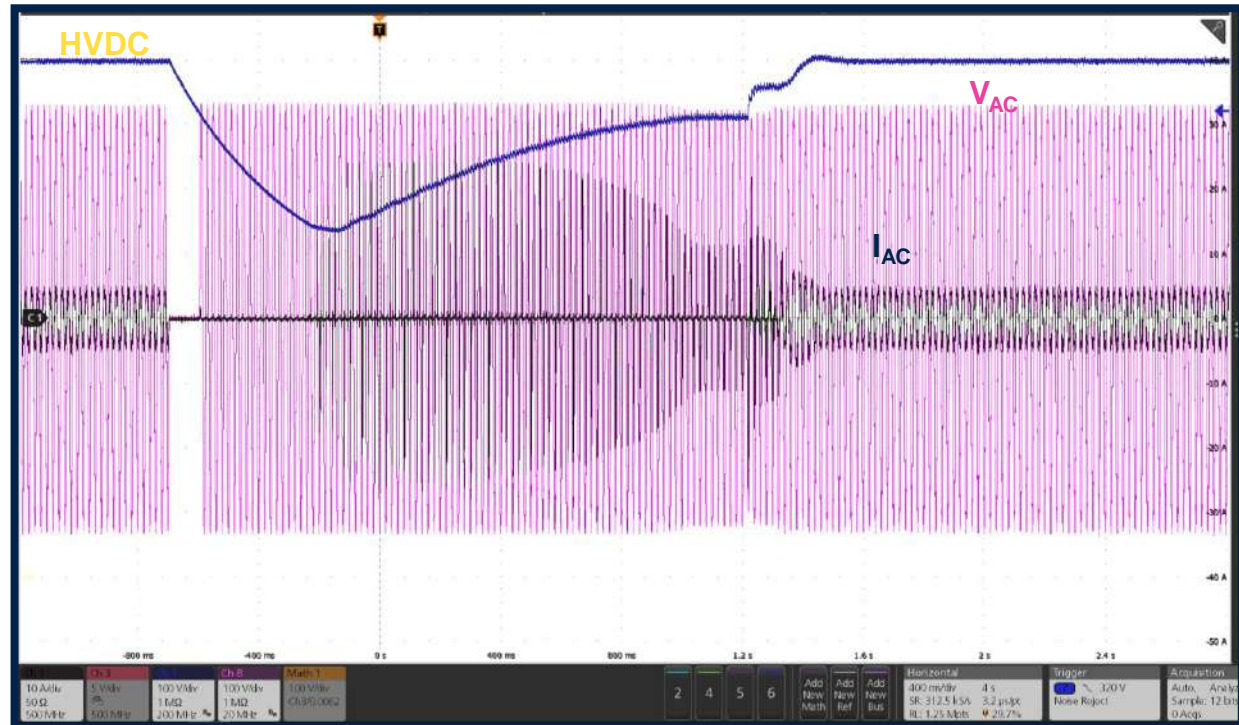AC line voltage interrupt lasts more than 30ms
SCRs are controlled back in soft-start when the VAC is reapplied, criteria B





Evaluation board performance

Main figures

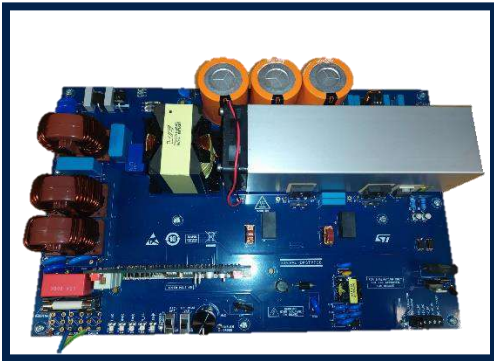

- Input AC voltage: 85VAC up to 264VAC
- Input AC frequency: 45Hz up to 65Hz
- DC output voltage: 400VDC
- Switching frequency: 72 kHz
- Maximum input current: 16 A RMS (POUT = 3.6KW)
- A high efficiency: > 97,5%
- A low THD distortion lower than 5 % of maximum
- Compliant to :
 - EN 55022 and IEC 61000-4-11 and IEC 61000-3-3
 - IEC 61000-4-5 surge: 4kV
 - IEC 61000-4-4 EFTY burst : criteria A @ 4kV
- Cooling: forced air cooling with active fan
- Design for operation with DC/DC converter
- Peak inrush current tuning
- Remove two bulky relays and an NTC resistor thanks to SCRs progressive start-up

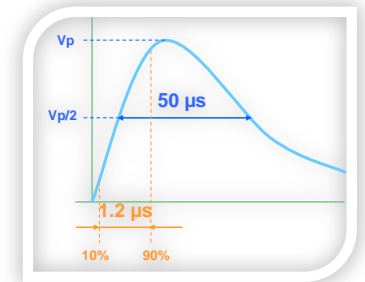
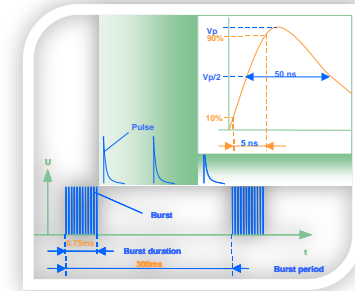


Agenda

- ST AC-DC inrush current limiter solutions
- PFC totem pole topology using SiC MOSFETs and thyristors
- Evaluation board performance
- **Takeaways**

Takeaways

- This presentation described a 3,6kW bridgeless totem pole PFC evaluation board for telecom and industrial applications with an digital Inrush current limiter using SiC MOSFETs and Thyristors.
- The Evaluation board design includes
 - A power board bridgeless totem pole boost with an inrush limiter circuit, SiC MOSFET and SCRs switch drivers and an auxiliary power supply
 - A control board with its MCU, a PFC/ICL control firmware
 - An adapter board for software debug

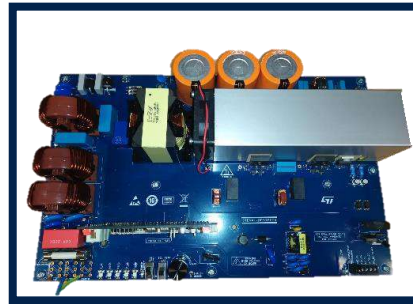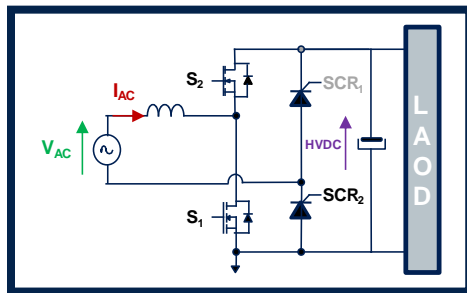

DC/DC or motor inverter can be connected to this evaluation board

- Evaluate a full ST solution
 - SCRs: To control the inrush-current to charge a DC bus capacitor and to fulfill with the IEC 61000-3-3 standard
 - SiC MOSFETs: To reduce passive components size and to provide a PFC with a very high efficiency thanks to low reverse recovery diode body
 - STGAP2S driver: Dedicated and optimized to control SiC MOSFETs
 - STM32 microcontroller: Embedded the PFC control algorithm

Takeaways

- Check the stand-by losses
 - Reduce drastically the stand-by losses of the traditional NTC/PTC Inrush-current limitation
 - Disconnect the DC bus capacitor from the AC mains when it does not have to operate
 - Without requiring a relay to be added to open the circuit during stand-by
- Check EMC
 - Immunity to fast transient and surge voltages
 - Common mode noise
- This reference design offering:
 - A high efficiency: $> 97,5\%$
 - A low THD distortion lower than 5 % of maximum load
 - A high switching lifetime with reduced EMI emissions
 - A robust circuit that meets EMC standards up to 4 kV
- SCR allows achieving a smart inrush current limitation at power up or line drop recovery compare to the traditional NTC and relays solution



Thank you

© STMicroelectronics - All rights reserved.

ST logo is a trademark or a registered trademark of STMicroelectronics International NV or its affiliates in the EU and/or other countries.

For additional information about ST trademarks, please refer to www.st.com/trademarks.

All other product or service names are the property of their respective owners.



life.augmented